

About

The mbhp DIN module is the unit that takes the inputs from a switch or encoder and sends this information to be processed by the [mbhp core module](#). It comes with multiple serial registers 74HC165; every register provides 8 digital inputs, which are sampled with the latch enable signal LD and shifted out with the clock signal CLK. The advantage of using such shift registers is, that they can be cascaded to a long chain without the need of more than 5 cables to the core module. The DIN board has been designed on a way which allows to cascade not only the ICs on the board, but also several DIN modules. But note that it depends on the firmware how much inputs are processed by the core module. For instance, the MIDIbox64 allows to connect up to 64 buttons = 8 ICs = 2 * DINX4, the MIDIO128 supports 128 inputs = 16 ICs = 4 DINX4 modules.

Getting Started

- [Preparation](#)
- [soldering](#)
- [Where to buy Parts](#)
- [etching_pcbs](#)
- [terminating_cables](#)

Special Instructions

- [smd_soldering](#)
- etc

Details

Pins

[DIN & DOUT pin table](#)

PCB files

```
list 'em
```

Schematic

```
you can do it
```

List of parts

list

Building it

Building instructions

blah blah blah

Testing

testing instructions


Common issues / Troubleshooting

blah blah blah

Reference

troubleshooting

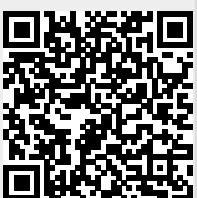From:
<http://midibox.org/dokuwiki/> - **MIDIbox**



Permanent link:
<http://midibox.org/dokuwiki/doku.php?id=home:mbhp:module:din&rev=1228208071>

Last update: **2008/12/02 08:54**