2025/11/14 13:11 1/2 Line Transmit

# **Line Transmit**

A slightly more compact version of the MBHP Line Driver Transmitter.

### **Schematic**

#### MBHP Transmitter.

The two obvious differences are the J3 jumper (disconnects +5V from being sent) and the addition of a 100mil header. This way a DB-25 connector (or something else?) with ribbon cable mounting could be mounted off-board and connected to the line driver with an IDC.

### **BOM v1.0**

Туре	Qty	Value	Package	Parts	Mouser	Reichelt	Conrad	Other	Notes
Resistors									
	0 (2)	100R 5%	ТНТ						not really needed
Capa	citor	S							
	2	100nF	THT 2.5mm	C1, C2					
ICs									
	2	MC3487	DIP16	IC1, IC2					
IC so	ckets	5							
	2		DIP16						
Head	lers								
	2	1*2	male						
	1 (0)	1*3	male						
	2	2*5	male						
	0 (1)	2*13	male						
Sock	ets								
	1 (0)	DB-25	female		806-KCDX-5S-S2				
Hard	ware	1							
	0 (3)	M3 spacer							optional, suggest to panel mount

## **Versions**

v1.0: first release.

## **Assembly**

Building is straightforward, just decide on whether CONN1 is the typical DB-25 or a pin header.

### License

Currently the design is  $\ \odot$  2017 antilog devices with all rights reserved; all documentation is CC BY-NC-SA 3.0.

From:

http://midibox.org/dokuwiki/ - MIDIbox

Permanent link:

http://midibox.org/dokuwiki/doku.php?id=wcore\_line-transmit&rev=1505167622

Last update: 2017/09/11 22:07

