

MIDIbox Matrix - MIDI Matrix with 56 Inputs and 56 Outputs

This MIDIbox implements a 56-port MIDI matrix/router using a core board and an FPGA-based add-on board together with a set of break-out boards and modules that allow for physically placing your MIDI ports where you actually need them.

Overview

Because my Waldorf Midibay became too small for connecting all of my MIDI equipment I had to design my own MIDI matrix / programmable patchbay. The modular MIDIbox Matrix has up to 56 input and 56 output ports and can be scaled to your requirements.



The prototype of the user interface (UI) already shows the main usage paradigm: a rotary encoder (on the lower right) is used to select the out port, thereafter the in port is selected with the rotary encoder on the left. This selection is confirmed by pressing the encoder. More changes to the current routing can be made, and when pressing the lower right rotary encoder, all changes are made effective and the routing is changed.

The buttons and encoder in the upper row, just below the display, belong to the SCS based menu system and will enter the config pages. Here, you can also load and save “patches” and configure the two mergers. The lower row of buttons doesn't do anything, except for one which is used for triggering a PANIC function, sending note off messages on all MIDI channels to all out ports.

MIDIbox Matrix features break-out boxes (BOBs) that give access to 4 in and 4 out ports at a time. These are connected via 9-pin serial cables to the main unit and are designed to be conveniently placed in the back of your rack, e.g. attached to the inner sidewall of a rack enclosure with screws or velcro tape. This means that instead of running 8 MIDI cables to the MIDIbox Matrix in order to connect four synths, you only need a single, cheap serial cable from your side rack to the center point of your matrix. I have successfully tried chaining five 5m long serial cables, bridging a total distance of 25m. It doesn't look as if this was the limit, though, and even larger distances between matrix and BOBs should be possible.

Two BOBs each connect to a single I/O board, which does all the level shifting and signal refreshing. Up to seven I/O boards can be attached to the heart of the MIDIbox Matrix, an FPGA-based switching and routing logic that is controlled via a core board such as the STM32 or the LPC17.

As the system is highly modular, it is possible to start with a low port count (4) and then increase the number of available ports by simply adding I/O boards and BOBs as needed. Fully loaded, i.e. offering 56 input and 56 output MIDI ports, the MIDIbox Matrix consists of

- 1x FPGA board
- 7x I/O boards
- 14x BOBs

plus a core board and the PCB holding the user interface.




BOB

The BOB is designed to be mounted against the inner wall of a 19" rack case. It connects via a shielded 9-pin serial cable to the main unit. On the BOB, the 9-pin DSUB socket is male, whereas a female DSUB socket is used on the main unit for protection against touching the pins (and the static-

sensitive ICs on the I/O boards in the main unit). As the serial cables are male/female ones, a connection can easily be extended by chaining cables (but beware that there is a limit with respect to how many single cables you can chain, due to increased contact resistances).

All MIDI in ports are located on one side, all MIDI out ports on the opposite side. They are clearly marked with the corresponding port numbers. I am using Formulor / Ponoko to laser cut the BOB's case, and the next one will therefore obviously be engraved 5...8, and so forth. A LED indicates whether the BOB is properly connected to the main unit. It discretely shines through the matte finished plexiglass case.

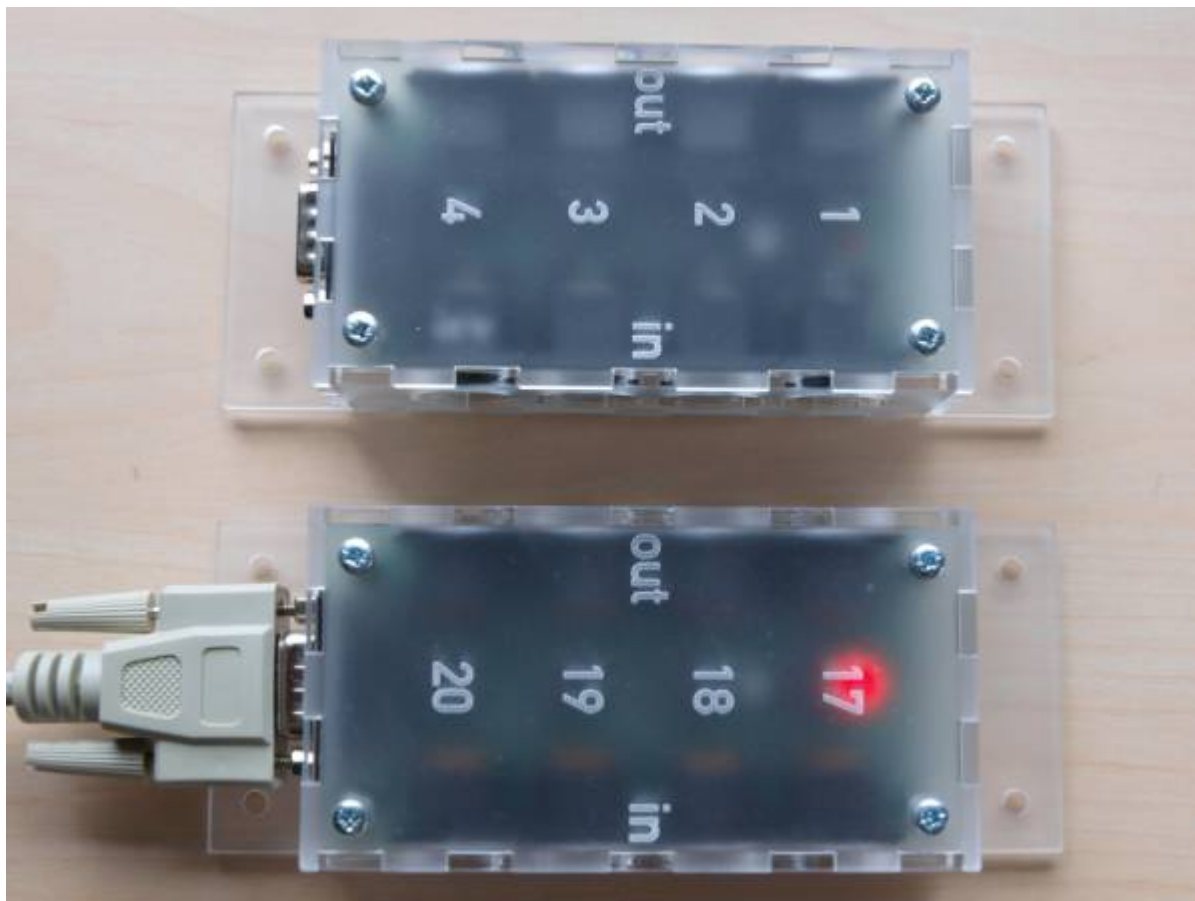

Like every MIDI device, MIDIbox Matrix features optocouplers on the MIDI in ports. Here, these optocouplers are located inside the BOB. This also means that the incoming MIDI signals are refreshed before they are passed on to the main unit. The optocouplers used here are standard 6N138 types and they are socketed for easy replacement (yes, optocouplers can break). Located on the soldering side of the BOB PCB are a number of SMD resistors in 1206 size. There is simply not enough real estate for more through hole components on this board.



Because I like the idea of recycling components that have barely been used in other, now obsolete

equipment, the MIDI sockets can also be replaced with DIN sockets bearing different kinds of footprints and/or additional pins. I frequently use 8-pin DIN sockets de-soldered from old video equipment as they are fully compatible with the 5-pin MIDI plugs. Of course, the standard 5-pin MIDI socket footprint will fit here as well!

Most DIN sockets have two little holes on the bottom side which can be used to apply a pair of screws to secure them to the PCB from underneath. The BOB's PCB has the corresponding holes, so for minimum mechanical stress screw your sockets!

It is also possible to use the BOB directly together with the STM32F4 core board. A single BOB can replace two I/O boards. The only additional thing required for this to work is an adapter or cable from D-SUB to the polarized strip connector J11E.

Schematic

No surprises here, we are using the standard MIDI schematics for 5V signal levels, including optocouplers in the MIDI In section: this is the [schematic of the BOB](#). The LED on this board is there to indicate that the BOB is active - it should light up if the BOB is properly connected to an I/O board.

Layout

The layout is governed by the basic design idea of having a *compact* little box that can easily be mounted in the back of a rack case. As a result it was necessary to use surface mounted resistors. However, this is no big deal - these are easily soldered after some practicing.



The total size of the PCB is 100mm x 50mm.

BOM

Reference	Description	Package	Value	Quantity	Mouser	Reichelt
C1	capacitor	C1V5	100µF	1		RAD 105 100/35
C2	capacitor	C1	100n	1		Z5U-2,5 100N
D1, D11, D21, D31	diode	D3	1N4148	4		1N 4148
R1, R4, R5, R11, R14, R15, R21, R24, R25, R31, R34, R35, R50	1/4W resistor	SM1206	220	13		SMD 1/4W 220
R2, R12, R22, R32	1/4W resistor	SM1206	1k	4		SMD 1/4W 1,0K
R3, R13, R23, R33	1/4W resistor	SM1206	4k7	4		SMD 1/4W 4,7K

Reference	Description	Package	Value	Quantity	Mouser	Reichelt
P1, P2, P11, P12, P21, P22, P31, P32	MIDI socket	DIN 5		8		MABP 5S
U1,U11,U21,U31	optocoupler	DIP-8	6N138	4		6N 138
U1,U11,U21,U31	IC socket	DIL-8		4		GS 8
LED1	LED	3mm	red	1		LED 3MM RT
P9	D-SUB 9pin male socket	DB9MC		1		D-SUB ST 09US
	D-SUB 9pin serial cable 5m			1		AK 261

All resistors are placed on the backside of the PCB. All other components are sitting on the front!

STM32F4-to-BOB Adapter

It is also possible to use a BOB directly together with an STM32F4 core board. Especially if you need the MIDI ports at some physical distance from the core board you should use the BOB-to-STM32 adapter. It provides an adapter from the IDC connector J11E on the core board to the DSUB 9pin connector on the BOB, as well as a line driver and level shifter for the MIDI out signals coming from the core board.



I/O Board

The I/O Board is the physical interface between the 5V MIDI signal level found in the BOB, and the 3.3V signal level required by the FPGA. This level shifting is done by one 74HCT541 and one 74LVC541 octal buffer / line driver, respectively. Especially the LVC version seems to be available in SMD only, hence a bit of SMD soldering is required here as well.

In addition to the 74xxx541 buffers, another pair of 74HC244 octal buffers / line drivers is used as input protection. These are socketed DIP ICs that can easily be replaced, should you ever connect an inappropriate signal to the DSUB jacks. Female DSUB sockets are used to protect the I/O Board against touching any I/O pins.



Each I/O Board handles 8 MIDI ins and 8 MIDI outs, i.e. it can connect to up to two BOBs.

Schematic

The v1.1 schematic of the MIDIbox Matrix I/O board can be downloaded [here](#).

Layout



The overall size of the PCB is 50mm x 80mm.

BOM

Reference	Description	Package	Value	Quantity	Mouser	Reichelt
C1, C2, C3, C4	capacitor	SM1210	100nF	4		X7R-G1206 100N
C5	polarized capacitor	radial	470µF	1		RAD 470/16
C6	polarized capacitor	axial	10µF	1		AX 10/35
U1	octal buffer / line driver / level shifter	SO20	74LVC541	1	595-SN74LVC541ADWR	
U2	octal buffer / line driver / level shifter	SO20	74HCT541	1	595-CD74HCT541M96	

Reference	Description	Package	Value	Quantity	Mouser	Reichelt
U3, U4	octal buffer / line driver	DIP-20	74HC244	2	595-SN74HC244N	74HC 244
U5	voltage regulator	TO92	TS2950	1		TS 2950 CT33
P1	IDC connector	13x2	IDC angled	1		WSL 26W
P2, P3	D-SUB 9pin female socket	DB9		2	649-D09S33E4PA00LF	D-SUB BU 09US
U3, U4	IC socket	DIL-20		2		GS 20

FPGA Board

The FPGA Board is the heart of the MIDIbox Matrix, as it performs the actual routing of MIDI ports. It is controlled via the DMA driven SPI port on the (STM32 or LPC17) core module, i.e. it connects to J8/J9, the serial DIN/DOUT ports.

The basic idea is rather simple: for each MIDI out port, a MIDI in port is selected whose signals should be forwarded. This selection is communicated to a 56(64)-to-1 multiplexer via a single 6(8)-bit shift register in the DOUT chain. Indeed, as we have 56 MIDI out ports, the corresponding DOUT chain is 56 shift registers long. However, thanks to the fact that this is “virtual” logic inside the FPGA, such long shift register chains do not present any signal integrity problems as witnessed in some other projects that use long SR chains. Any other DIN or DOUT shift registers you might want to use, e.g. for the user interface, must be located in the SR chain *before* this board.

Additionally, you can also merge MIDI streams. The FPGA board holds two PIC16(L)F88 based 2-to-1 MIDI mergers in parallel. Their inputs are served from any of the 56 MIDI in ports, and their outputs are forwarded to the STM32 core board for further MIDI stream processing. These streams can then be fed back into the Matrix and routed to any of the 56 MIDI out ports.



On the left is a rendering of the FPGA board created with KiCAD. This is the second generation v1.1 FPGA board which has a pair of MIDI I/Os, and an AC power plug (which can also be used to feed DC power). The board can loop through the USB signals from the Micro USB plug found on the STM32F4 Discovery (core) board to the outside world when the whole unit is mounted in an enclosure. The FPGA board connects to J8/J9 of the core board for DIN and DOUT chains, and to J11E for MIDI connectivity. The pair of MIDI I/O sockets on this board connects directly to MIDI I/O number 4 of the core board. In the future, it might be possible to remote control the MIDIbox Matrix via this MIDI port (yes, if my time allows...).

The FPGA board provides a range of power supply options. It can be fitted with a 5V and a 3.3V power section - the latter is obligatory if you want to use one or two PIC16LF88 MIDI mergers running at 3.3V. You can also feed them 5V, in which case the 3.3V power section can be omitted, as the FPGA gets its 3.3V from its own 3.3V regulator. Also, you might have a stable 5V supply already. Then, you can also omit the 5V section. You can also supply the core board from the FPGA board via J8/J9 and

J11E.

The actual FPGA sits piggyback underneath the PCB, on a separate daughter board. An Altera Cyclone II device is used (EP2C8) which has a sufficiently large number of I/O pins. The daughterboard is from [Waveshare](#), a Chinese manufacturer offering a wide range of development and evaluation boards.

Schematic

coming soon

Layout


coming soon

BOM

coming soon

User Interface

The user interface (UI) is based on the [MIDIbox SCS](#), two dedicated clickable encoders for in- and out-port selection, and an additional PANIC button. It fits in the frontpanel of a standard 2U rack case, offers a 2x24 display for feedback, and 5 buttons along with an encoder for navigating the menu system. So far, an alpha prototype version of the board has been tested successfully on veroboard.

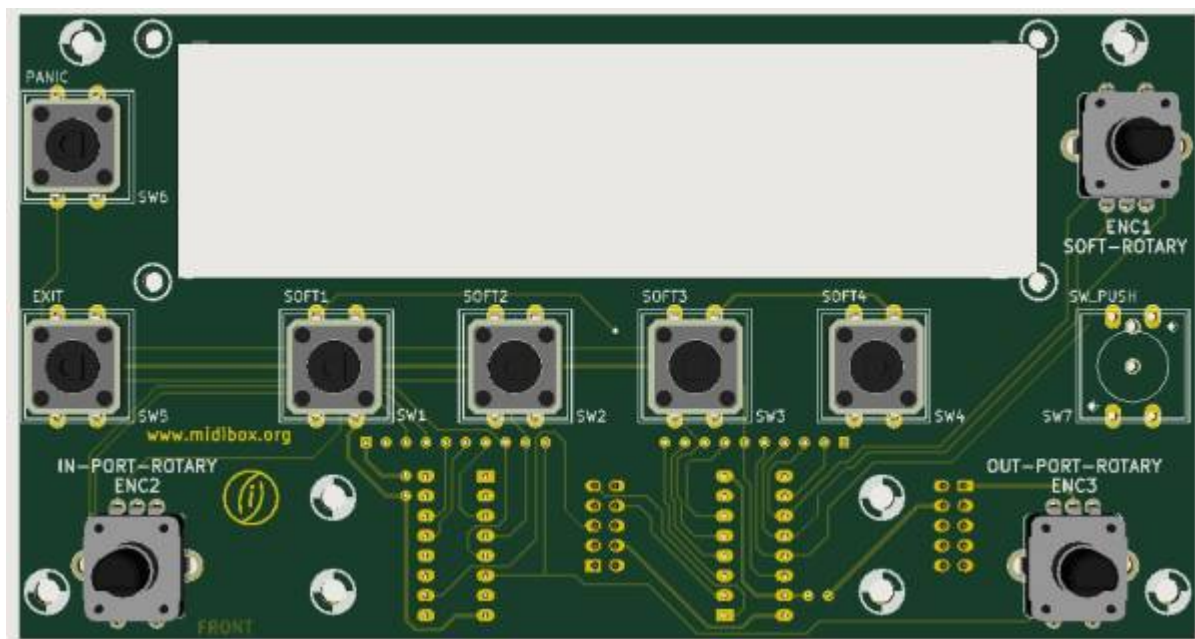

A second generation PCB as modeled above will be ordered soon. This PCB can also be used with other projects involving an SCS, e.g. the [MIDIbox NG](#). Both, my favourite switches from [Marquardt \(6425 series\)](#), as well as the [E-Switch TL1100 series](#) (see e.g. MB SEQv4) can be used.

From:

<https://midibox.org/dokuwiki/> - **MIDIbox**

Permanent link:

https://midibox.org/dokuwiki/doku.php?id=mb_matrix&rev=1402841984

Last update: **2014/06/15 14:19**

