

# wCoreF4 PCB

This is the carrier board for the Waveshare Core407v. It performs breakout functions of all of the standard ports as per the design based on the STM32 Discovery.

## Schematic

The circuit is mostly identical to what was drawn previously. The following parts are different:

### USB entry (J1)



This header supplies +5V, 0V, USB data and the ID state. Normally it will be connected to the [USB module](#) by a short cable.

### Extended port (J16E)



The original J16 functionality is preserved, but extra pins are available on an IDC16 header. These include the Reset signal and pins normally controlling LEDs. This header is normally connected to the [RES-SD module](#).

### User button (JPA0)



This jumper replaces the “bootloader” functionality of the Discovery board's blue button. It could be wired to an external panel control if needed.

## BOM v1.0

Type	Qty	Value	Package	Parts	Mouser	Reichelt	Conrad	Other	Notes
<b>Resistors</b>									
	1	330R 5%	THT	R102					
	4	1k 5%	1206	R7B1-4					
	2	1k 5%	THT	R11, R13					
	2	2k2 5%	THT	R7A, R8A					
	2	2k2 5%	1206	R7B, R8B					
	1	10k 5%	THT	R12					
	1	220k 5%	THT	R101					
<b>Pots</b>									
	2	10k	6*5mm vert	P1, P2					
<b>Capacitors</b>									
	3	100n	1206	C1A, C1B, C2					
<b>Diodes</b>									
	1	1N4148	THT	as marked					
<b>Transistors</b>									
	1	BC337	TO-92	T1					
<b>ICs</b>									
	2	74HCT125	SOIC	IC1A, IC1B	595-SN74HCT125DR				Ensure <b>HCT</b>

Type	Qty	Value	Package	Parts	Mouser	Reichelt	Conrad	Other	Notes
<b>Resistors</b>									
	1	74HC595	SOIC	IC2					
<b>Headers</b>									
	2	1*2	male						
	1	1*3	male						
	1	1*5	male	J1					or wire directly
	9	2*5	male						
	3	2*8	male						
	2	2*25	female						solder before male headers
<b>Hardware</b>									
	4		M3 spacer	8mm(?)					
<b>MCU breakout</b>									
	1	Waveshare Core 407v							

## Versions

v1.0: first release.

## Assembly

The following build order is suggested:

- R7B1-4 (1k 1206) and located near J15\_S on the top side
- R7B and R8B (2k2 1206) on the bottom side
- C1A, C1B and C2 (100n 1206) on the bottom side
- IC1A, IC1B (74HCT125) and IC2 (74HC595) on the bottom side
- Top-side THT resistors R7A 2k2, R8A 2k2, R11 1k, R12 10k, R13 1k and diode
- Bottom-side THT resistors R101 220k, R102 330R
- Top-side transistor and trimpots
- Bottom-side JPA0 header
- Bottom-side 2\*25 pin female headers
  - for a SEQ v4+ build, consider omitting headers J4B, J5A, J5B, J10A, J10B and J18
- Top-side male headers, except for J1
- Solder J1 in conjunction with the [USB module](#)
- Mounting brackets if needed


## Connecting the Core407v breakout

- Checking the Waveshare board, you will see that there is a real-time clock crystal and associated caps connected across PC14 and PC15. I think it's best to remove these parts so

they don't interfere with normal operation. Clip the leads of the crystal and desolder the part if you like. The caps should come off quite easily with a soldering iron tip heating both pads. Don't leave any solder bridges!



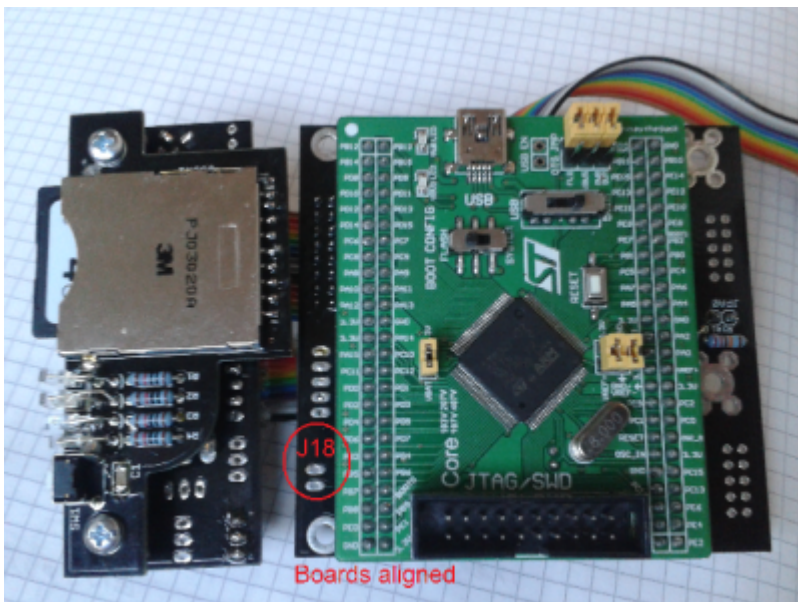- The Core 407v board plugs in on the bottom side with the the USB mini connector located below J4A.
- Explained another way: the JTAG header should be somewhat aligned with the 2-pin CAN header J18:



- The 407v board should not protrude past the edge of the PCB.
- Remove the OTG jumpers “FLG,” “VBUS” and “PWR OUT.” USB won't work properly with these closed.
- I believe that the correct state of the BOOT CONFIG switch should be set to “FLASH”
- There's another switch to select the +5V power. It should be set to “USB” when flashing the board using the USB mini connector as a power source, but for our purposes set it to “PWR 5V”.

## License

Currently the design is © 2017 antilog devices with all rights reserved; all documentation is CC BY-NC-SA 3.0.

From:

<https://midibox.org/dokuwiki/> - **MIDIbox**

Permanent link:

[https://midibox.org/dokuwiki/doku.php?id=wcoref4\\_pcb&rev=1530269434](https://midibox.org/dokuwiki/doku.php?id=wcoref4_pcb&rev=1530269434)

Last update: **2018/06/29 10:50**

