
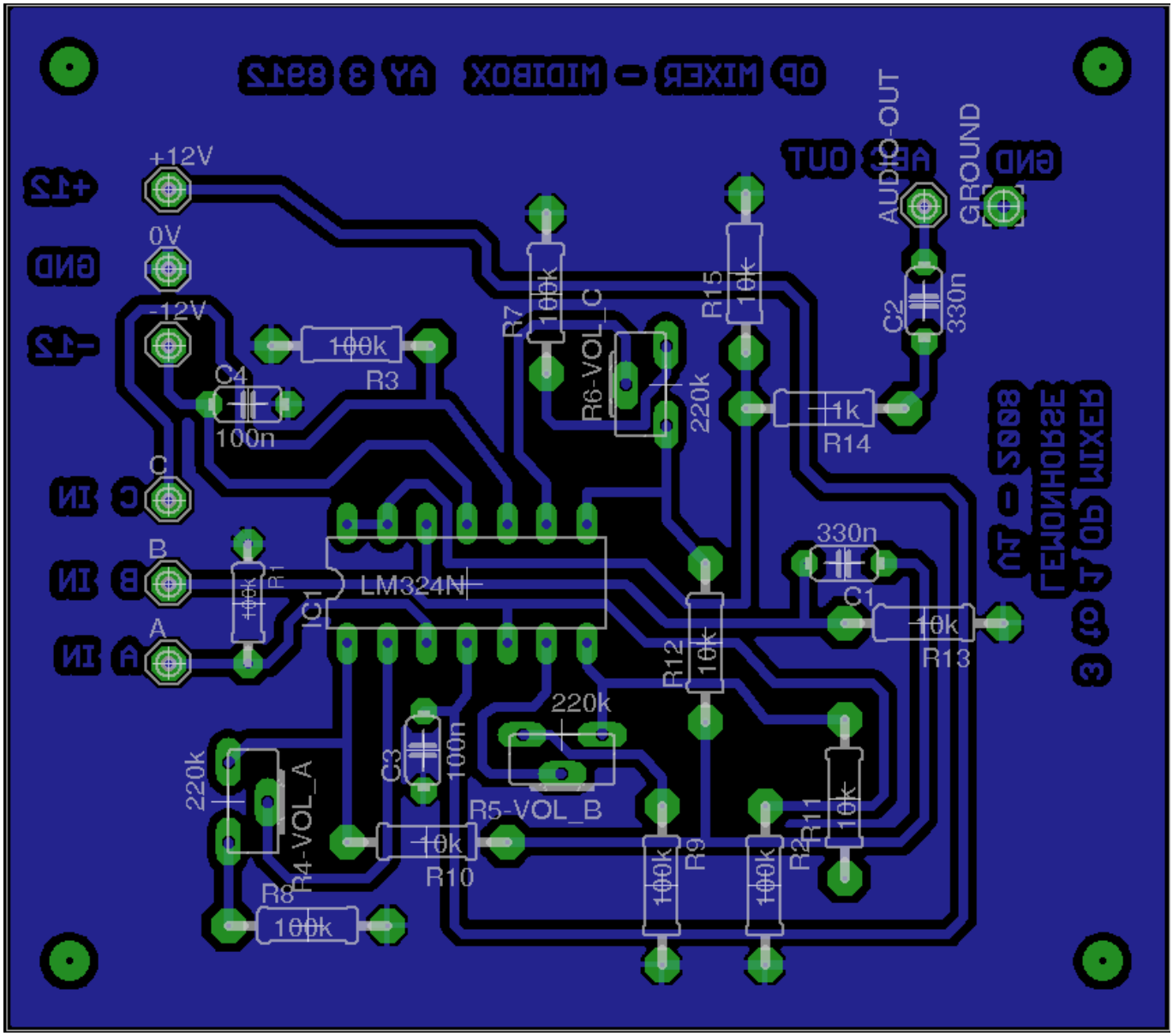
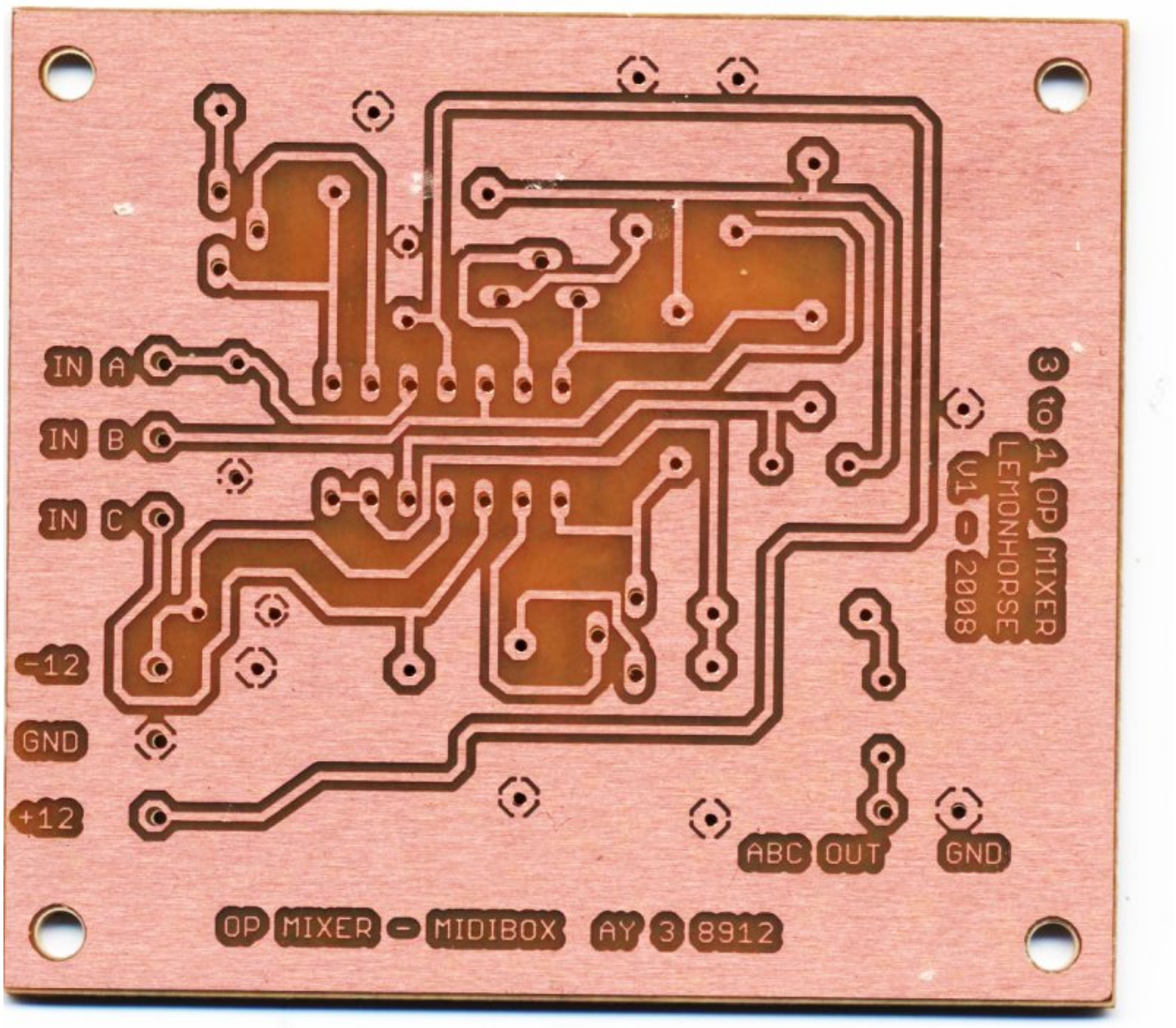
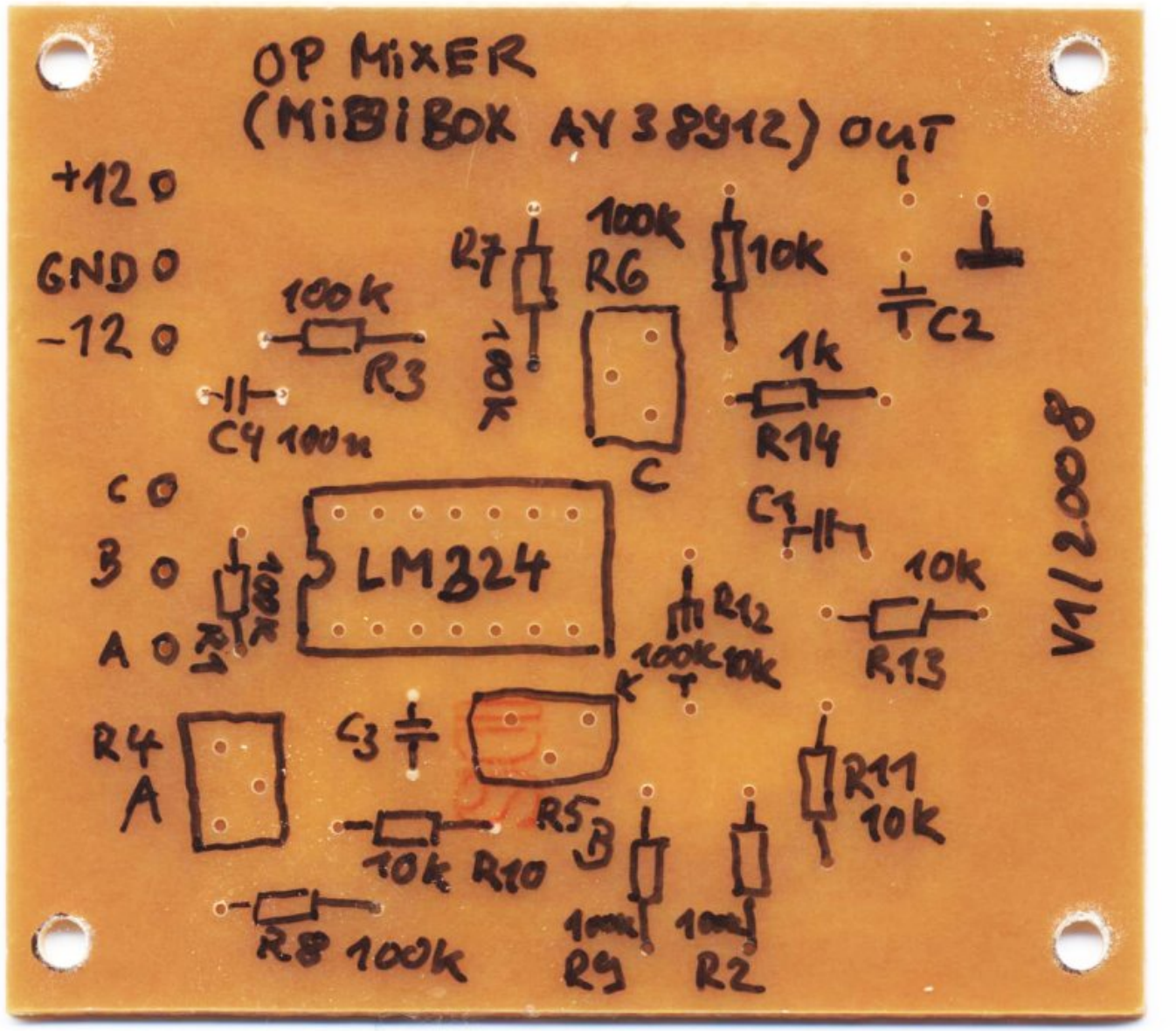
MIDIBox AY 3 8912 Mixer

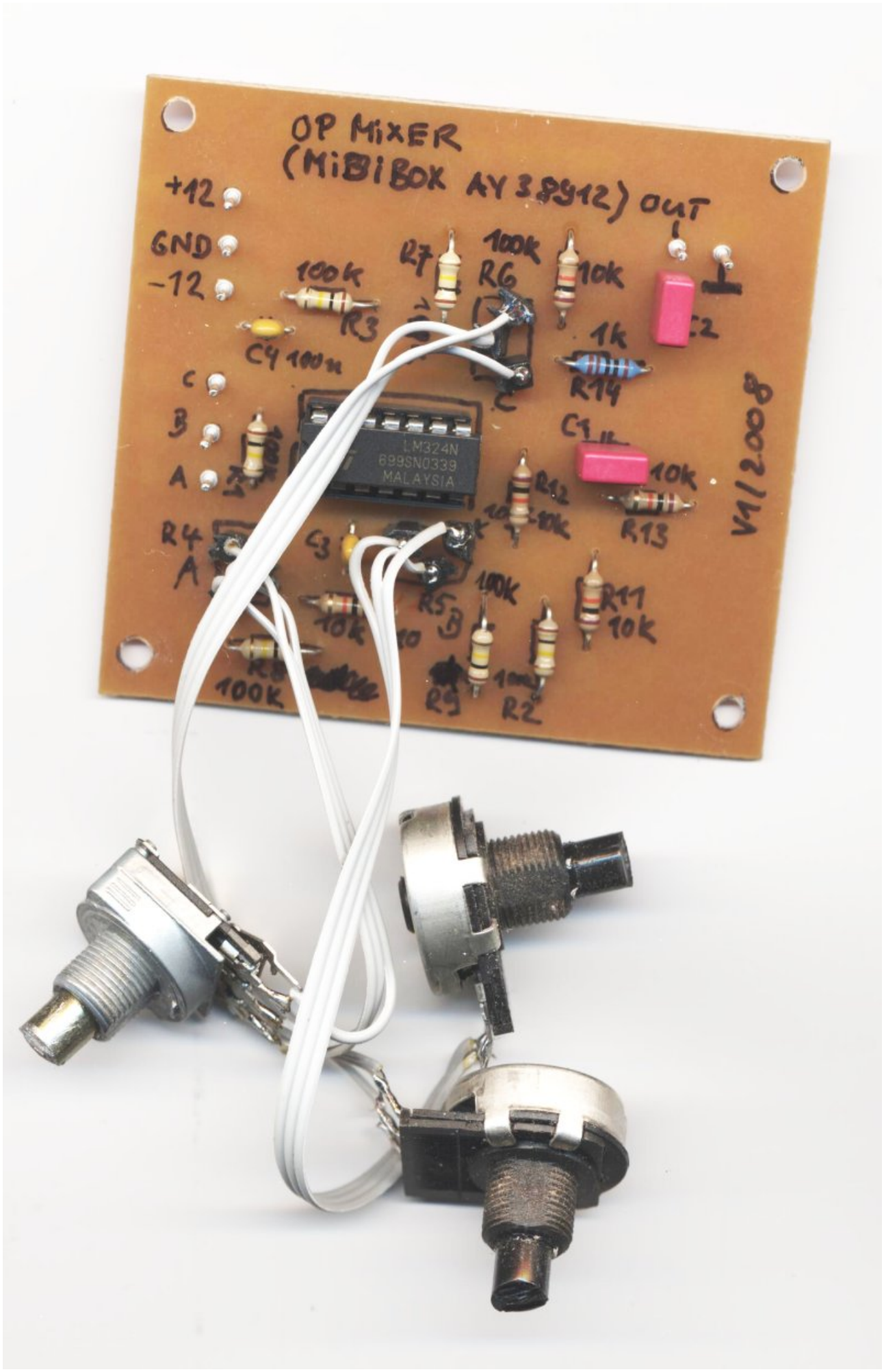
- OP AMP Mixer (Tone ABC) for the MIDIBox AY 3 8912 (Ver. 1a)




IN A
IN B
IN C
-12
GND
+12
ABC OUT
GND
OP MIXER - MIDIBOX AY 3 8912
3 to 1 OP MIXER
LEMONHORSE
V1 - 2008


OP MIXER
(MIDIBOX AY 3 8912) OUT
+12 O
GND O
-12 O
100k
R7
100k
R6
10k
C2
100k
R3
1k
R14
C4 100n
C
C O
B O
A O
LM324
C1
10k
R13
R12
100k
10k
R4
A
C3
R5
B
10k
R10
R11
10k
R8 100k
R9
R2
V1.2008

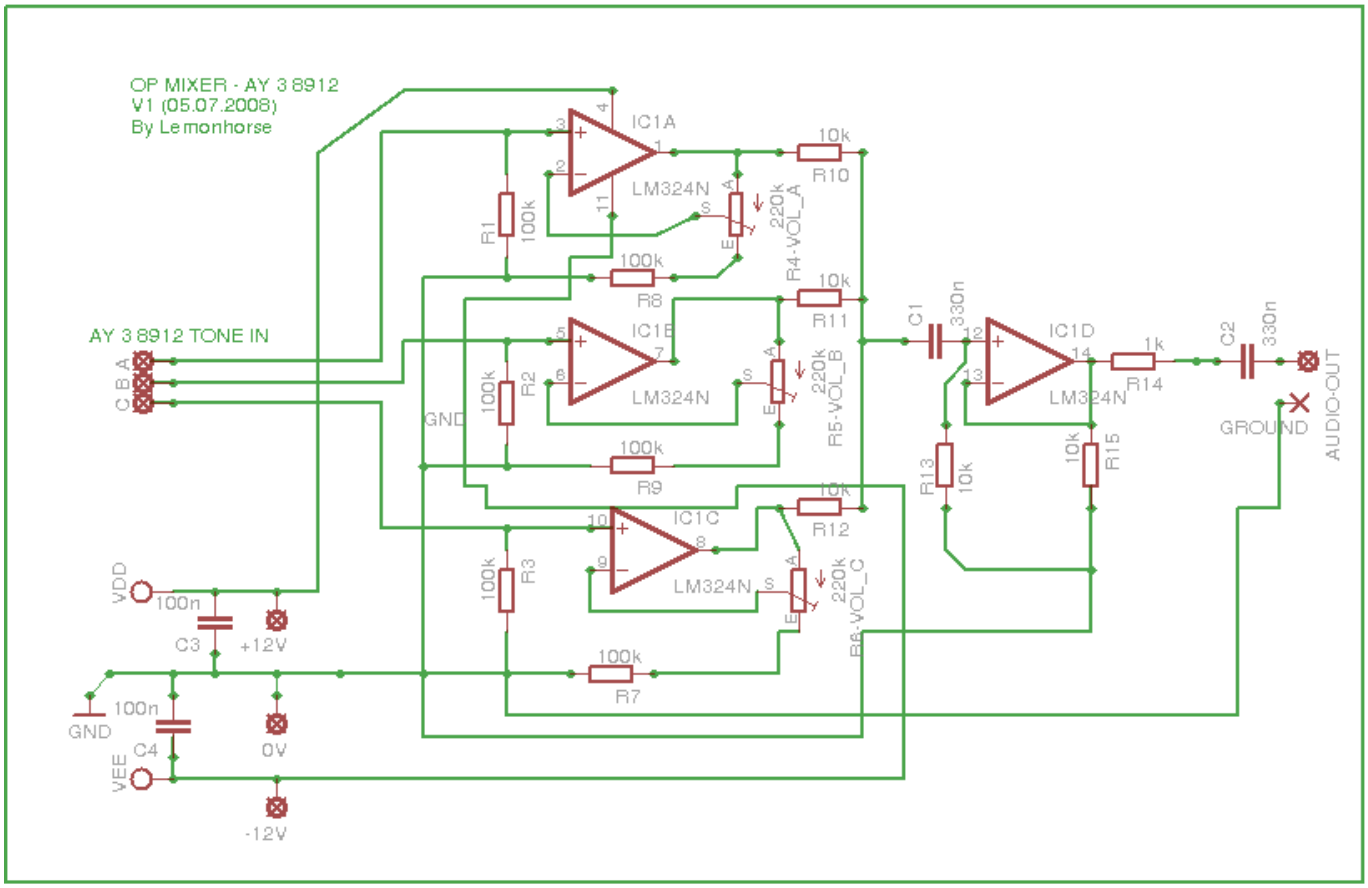
OP MIXER
(MIDIBOX AY 3 8912) OUT
+12
GND
-12
100K
R7
100K
R6
10K
C2
100K
R3
C4 100n
1K
R14
C
B
A
LM324N
699SN0339
MALAYSIA
R12
10K
R13
V1/2008
R4
A
C3
100K
R5
B
10K
R11
10K
100K
R9
R2



Notes:

- Pot R4 (Volume Tone A), R5 (Volume Tone B) and R6 (Volume Tone C) are designed for volume finetuning (not for turning off tone A/B/C)

Pot Options:

- R4, R5, R6 = 100k (less volume)
- R4, R5, R6 = 220k (more volume)

OP: LM324N (4xOP, +/-12V) - Datasheet:


- ⇒ LM324N.pdf /
- ⇒ lm324.pdf

Download: Eagle 5.1 Files + Partlist - MIDIBox AY 3 8912 Mixer (Ver.1a)

mbay_eagle.zip

::: :: :


MASTER VOLUME POT

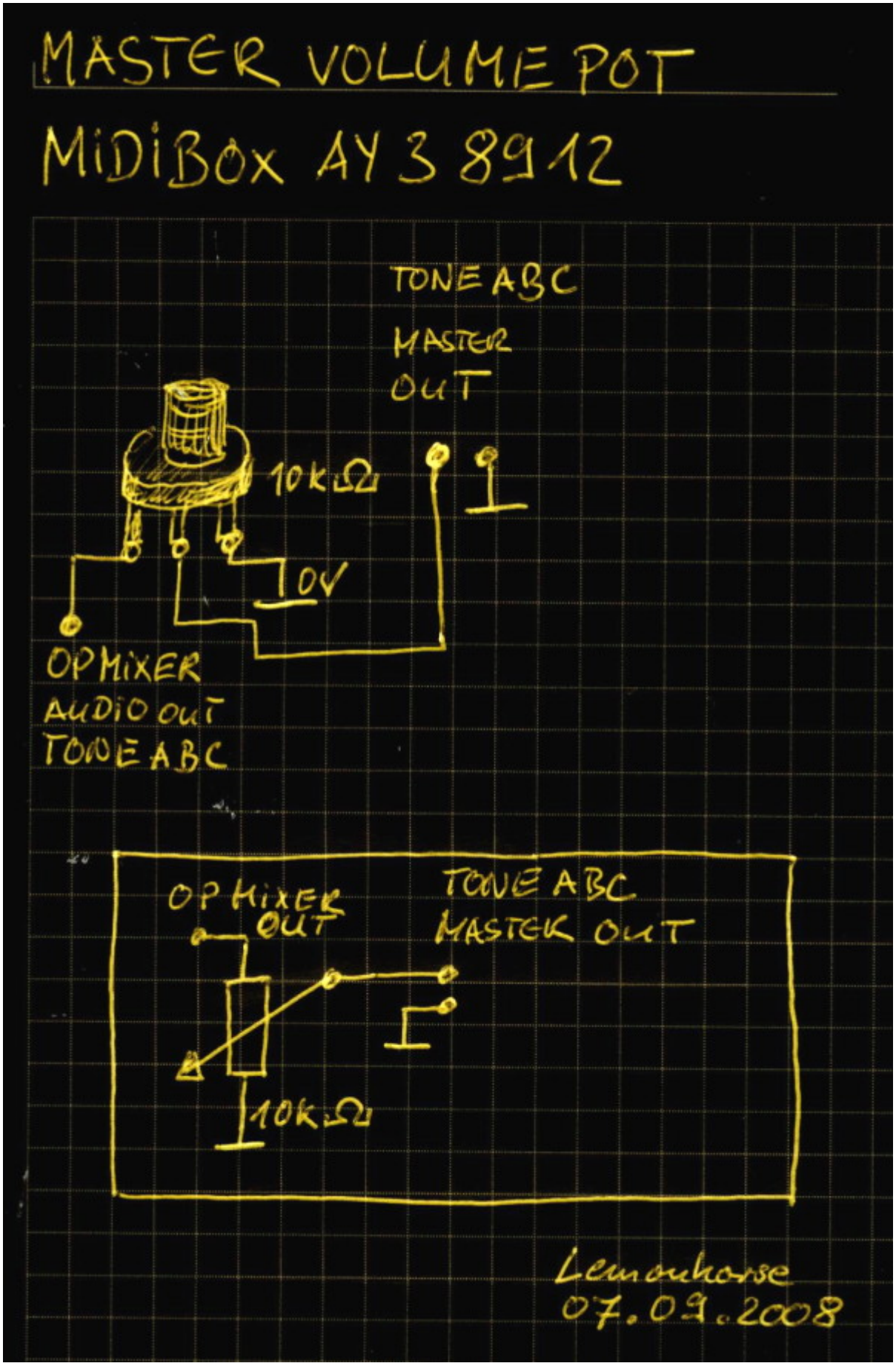
MASTER VOLUME POT
MIDIBOX AY 3 8912
TONE ABC
MASTER
OUT
10KΩ
0V
OP MIXER
AUDIO OUT
TONE ABC
OP MIXER
OUT
TONE ABC
MASTER OUT
10KΩ
Lemonhorse
07.09.2008

::: :: :

No OP MIXER Option

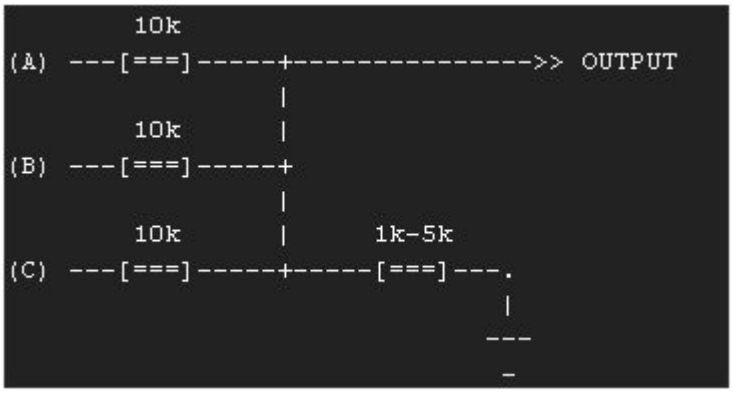Notice: “You can easily leave out the opamp buffer board for testing. Just connect all three outputs via 10k resistors and add a pulldown of 1k-5k from that signal to ground.” (nILS Podewski, 2008-10-02)



:::

::

:

PCB

The AY 3 8912 PCB and the AY 3 8912 OP-Mixer PCB are available at Mikes Onlineshop

http://www.mikes-elektronikseite.de/shop_englisch/index.htm

[26.09.2008]

From:
https://midibox.org/dokuwiki/ - **MIDIbox**

Permanent link:
https://midibox.org/dokuwiki/doku.php?id=midibox_ay_3_8912_mixer&rev=1225050072

Last update: **2008/10/26 19:41**