
BLM SCALAR FIX -Based on findbhudda's original design:
http://www.midibox.org/dokuwiki/doku.php?id=findbuddha

DESIGN SOFTWARE USED:
KiCAD for PCB/Schematics: http://kicad.sourceforge.net/wiki/Main_Page


---

KNOWN ISSUES / BUILD SUGGESTIONS:
- blm-scalar.* contain an error. Pins I4-I7 are mirrored. This is easily fixed with a connector modification, and the blm-scalar module seems to work as intended.
- blm-scalar v1.1 attempts to fix this error. Moved connectors J1, J2 & Resistor Net 1 to make room for corrections.

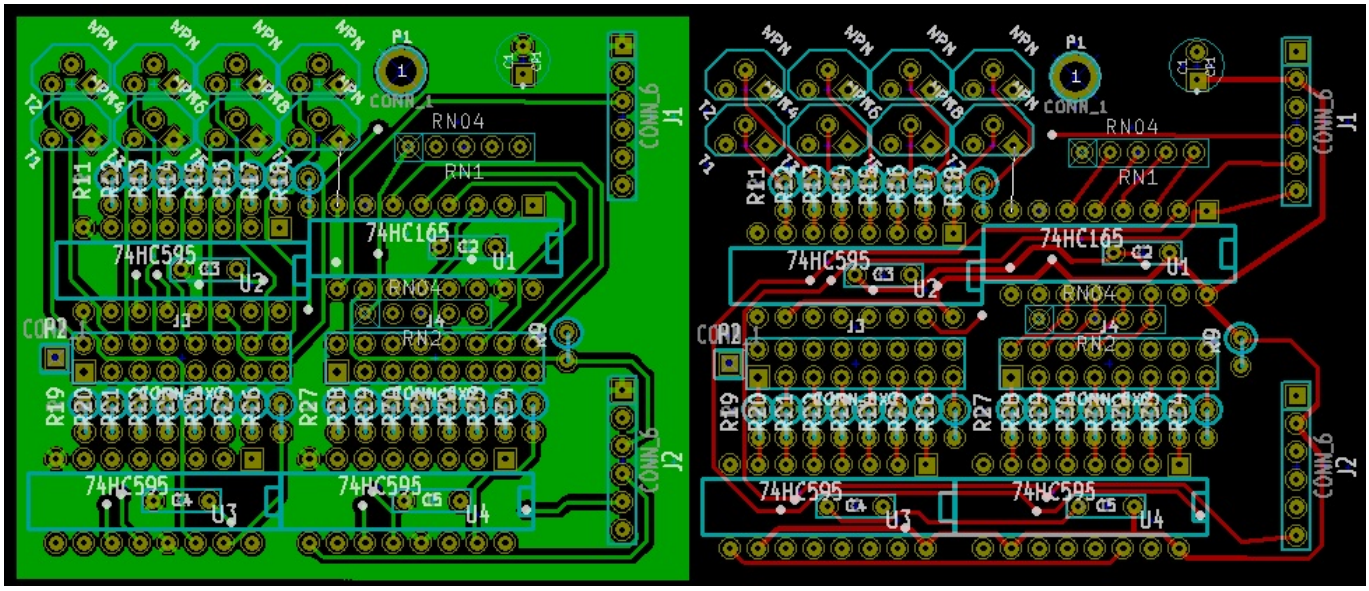DESIGN FILES:
Corrected blm-scalar v1.1.brd below & attached: blm-scalar_v1.1.zip



Original findbhudda board below:

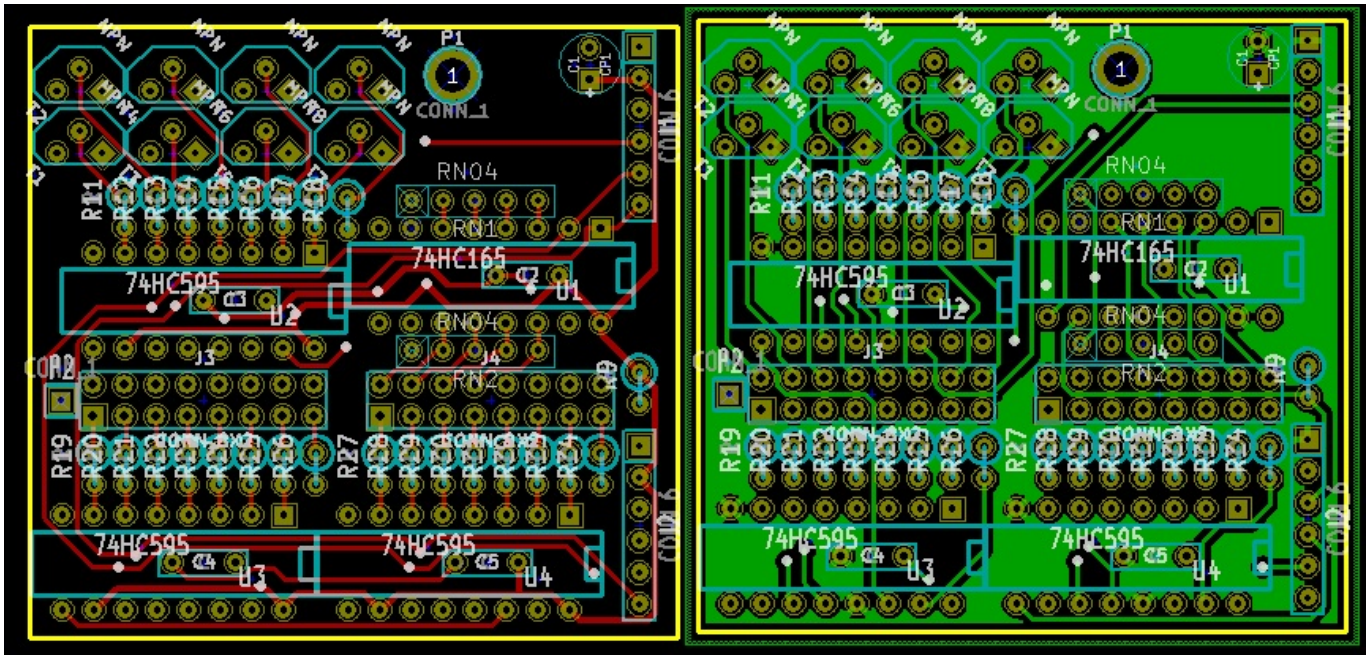

From:
https://midibox.org/dokuwiki/ - **MIDIbox**

Permanent link:
https://midibox.org/dokuwiki/doku.php?id=peterpressure&rev=1323663169

Last update: **2011/12/12 04:12**